

ENGR 212: Laboratory Experiment 2

Answer Guide & TA Notes

Teaching Assistant Reference

Overview

This guide outlines the theoretical values and expected behaviors for **Lab Experiment 2**. Use this to verify student results and explain discrepancies during the lab session.

1 Part 1: Voltage Divider Circuit Calculations

Problem Statement

Students must calculate v_{out} , i , and P_{R_2} for the circuit in Figure 1(a) with a fixed source of 10V and $R_1 = 10k\Omega$. The value of R_2 varies across five specific resistance values.

Formulas Used

The circuit is a standard unloaded voltage divider.

1. **Current (i):**

$$i = \frac{V_{source}}{R_{eq}} = \frac{10V}{R_1 + R_2}$$

2. **Output Voltage (v_{out}):**

$$v_{out} = i \times R_2 = 10V \times \left(\frac{R_2}{R_1 + R_2} \right)$$

3. **Power Dissipated by R_2 (P_{R_2}):**

$$P_{R_2} = i^2 \times R_2 = \frac{(v_{out})^2}{R_2}$$

Answer Key (Theoretical Values)

Use the table below to check the “Calculation” columns in student reports. Note that power is calculated in milliwatts (mW).

R_2 Value	Total R ($R_1 + R_2$)	Current i	Voltage v_{out}	Power P_{R_2}
2.2 k Ω	12.2 k Ω	0.820 mA	1.80 V	1.48 mW
4.7 k Ω	14.7 k Ω	0.680 mA	3.20 V	2.18 mW
10 k Ω	20.0 k Ω	0.500 mA	5.00 V	2.50 mW
20 k Ω	30.0 k Ω	0.333 mA	6.67 V	2.22 mW
33 k Ω	43.0 k Ω	0.233 mA	7.67 V	1.78 mW

Table 1: Theoretical values for Table 1. Measured values should be within resistor tolerance ($\approx 5\%$).

2 Part 2: LED Circuit Analysis

Theoretical Expectations

1. Forward Bias Behavior (Steps a–c)

- **Threshold:** An LED is a non-linear device. Current will remain near zero until the voltage across the LED reaches its **turn-on voltage** ($V_{turn-on}$).
- **Typical $V_{turn-on}$:** For a standard red LED, this is typically **1.8V – 2.0V**.
- **Behavior:**
 - **Input 1V:** Source < Turn-on. LED is OFF. $I \approx 0\text{mA}$. $V_{LED} \approx 1\text{V}$ (Open circuit behavior).
 - **Input 2V ~ 5V:** Source > Turn-on. LED turns ON. V_{LED} clamps near the forward voltage ($\approx 2\text{V}$) and rises very slowly. Current increases linearly with the remaining voltage drop across the resistors.

2. Effect of Varying R_1 (Step d)

Increasing R_1 increases the total series resistance ($R_{total} = R_1 + R_2$).

- **Impact:** For the same input voltage, a higher R_1 results in **lower current** flowing through the LED, making it dimmer.
- The voltage across the LED (V_{LED}) will remain relatively stable (characteristic of a diode), but the voltage drop across the resistors will change significantly.

3. Estimating Turn-on Voltage (Step f)

When students plot I (y -axis) vs V_{LED} (x -axis), they should observe a “knee” in the graph.

- The curve should be flat (at $I = 0$) until roughly **1.8V** (for Red LED), after which current shoots up steeply.

Sample Calculation

Assuming a Red LED ($V_{turn-on} \approx 1.9V$), Input = 5V, and $R_1 = 0\Omega$:

$$\begin{aligned}V_R &= 5V - 1.9V = 3.1V \\R_{tot} &= 3.9k\Omega \\I &= \frac{3.1V}{3.9k\Omega} \approx 0.79mA\end{aligned}$$

Supplementary Note: Loading Effect

Although “loading effect” is listed in the objectives, it is not explicitly calculated in the numbered steps.

- **Concept:** The loading effect occurs when a load resistor R_L is attached in parallel to R_2 (Figure 1b). This reduces the effective resistance of the bottom branch to $R_{eq} = R_2 \parallel R_L$.
- **Result:** The measured v_{out} will be **lower** than the calculated unloaded v_{out} from Table 1.