

Lab 2

Getting started with Ohm's Law, KVL, KCL,
and Multi-Meter Measurements

Student Name: Sean Balbale

Instructor: Dr. Iman Salama

Lab Partner Name: Krish Gupta

Date: September 9th, 2024

1 Introduction

The lab had a few primary purposes: practicing Ohm's law, KVL (Kirchhoff's voltage law), and KCL (Kirchhoff's current law), and learning how to use a Multimeter. The Keysight power supply and digital multimeter were used in this lab, which taught a necessary skillset for all electrical engineers.

2 Results

2.1 A Very Simple DC Circuit



Figure 1: Second Circuit built on breadboard. The red wires and rail are +6V while the black wire and blue rail are ground.

During this lab section, a very simple circuit (Figure 1) was built on a breadboard.

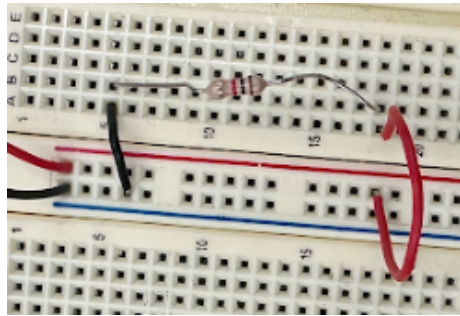


Figure 2: Second Circuit built on breadboard. The red wires and rail are +6V while the black wire and blue rail are ground.

Figure 2 shows the circuit that was built. The theoretical amperage flowing through the resistor can be calculated using Ohm's Law. This calculation is shown in Equation (1).

$$I = \frac{V}{R}, \text{ where } V = 5V \text{ and } R = 1k\Omega \quad (1)$$

The actual value of the resistor used was found to be $1.0004k\Omega$. When connected to a multimeter the voltage drop was measured to be $4.9986 V$. The loop current was measured to be $4.9942 mA$. The measured values were close to the calculated values, which is expected due to the accuracy of the equipment used. The discrepancy between the calculated and measured values can be attributed to the tolerance of the resistor and the accuracy of the multimeter. If the voltage over the resistor doubles then, so will the loop current.

2.2 KCL

3 Discussions and Conclusions

4 References

[1] Dr. Iman Salama. "Lab 2 – Getting started with Ohm's Law, KVL, KCL, and Multi-Meter Measurements" Northeastern University. 9 September 2024.