

ENGR 212 Laboratory Experiment 2

Group Lab Report

Objectives:

1. Build and test a voltage divider circuit.
2. Investigate the effects of loading on the voltage divider circuit.
3. Characterize the current-voltage relationships of an LED.

Materials:

1. One breadboard
2. One Agilent 34410A or 34401A digital multi-meter (DMM)
3. Resistors (100 Ω , 1 k Ω , 2.2 k Ω , 3.9 k Ω , 4.7 k Ω , 10 k Ω , 20 k Ω , 33 k Ω , 100 k Ω), LED, cables.

Construction of a Voltage Divider Circuit:

1. We will build the circuit diagram shown in Figure 1(a).

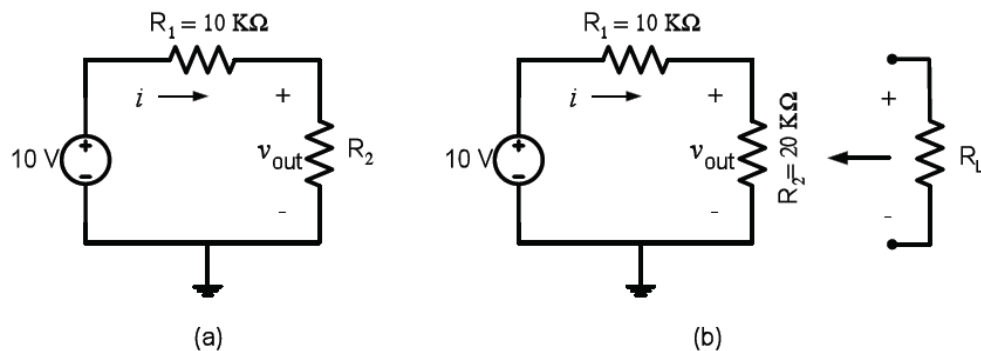


Figure 1

2. Calculate v_{out} , i , and P_{R_2} when R_2 is 2.2 k Ω , 4.7 k Ω , 10 k Ω , 20 k Ω , and 33 k Ω .
3. Construct the circuit in Figure 1(a) with the R_2 provided in step 2. Measure v_{out} and i using the DMMs as shown in Fig. 2; and then calculate P_{R_2} . Repeat for all R_2 values.
4. Tabulate your results from steps 2 (in the Calculation column) & 3 (in the Reading column) in the format shown in Table 1 for comparison.

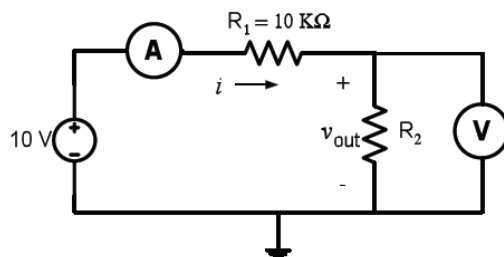


Fig. 2

Table 1

R_2	V_{out}			i			P_{R_2}		
	Calculation	Reading	Error (%)	Calculation	Reading	Error (%)	Calculation	Reading	Error (%)

$$\text{Error} = (\text{Calculation} - \text{Reading}) / \text{Calculation} * 100\%$$

A Simple LED Circuit:

In this part of the experiment we will experiment with a light emitting diode (LED). Construct the circuit shown in Figure 3. The longer leg of the LED represents a positive terminal. Be sure to connect the LED such that it is forward biased.

Measurements & Questions:

- Set the resistor R_1 in Figure 3 to $0\ \Omega$.
- Change the dc voltage from 1 to 5 volts with an increment of 1 volt. If you connected the circuit correctly, your LED should gradually turn on, ending with a bright red light.
- Measure and record the voltage across the LED and the current flowing through it using your multimeters for each value of voltage.
- Change R_1 to $100\ \Omega$, $1\ \text{k}\Omega$, and $100\ \text{k}\Omega$. With each setting of R_1 , repeat step b and c.
- Plot the measured current through the LED versus the measured voltage drop across the LED for a given value of R_1 .
- Estimate the turn-on voltage of the LED. (This will be the voltage at which the current is no longer zero.)

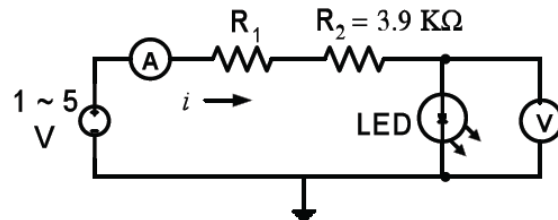


Fig. 3