

ENGR 212: Laboratory Experiment 2

Answer Guide & TA Notes

Teaching Assistant Reference

Overview

This guide outlines the theoretical values and expected behaviors for **Lab Experiment 2**. Use this to verify student results and explain discrepancies during the lab session.

1 Part 1: Voltage Divider Circuit Calculations

Problem Statement

Students must calculate v_{out} , i , and P_{R_2} for the circuit in Figure 1(a) with a fixed source of 10V and $R_1 = 10\text{k}\Omega$. The value of R_2 varies across five specific resistance values.

Formulas Used

The circuit is a standard unloaded voltage divider.

1. **Current (i):**

$$i = \frac{V_{source}}{R_{eq}} = \frac{10\text{V}}{R_1 + R_2}$$

2. **Output Voltage (v_{out}):**

$$v_{out} = i \times R_2 = 10\text{V} \times \left(\frac{R_2}{R_1 + R_2} \right)$$

3. **Power Dissipated by R_2 (P_{R_2}):**

$$P_{R_2} = i^2 \times R_2 = \frac{(v_{out})^2}{R_2}$$

Answer Key (Theoretical Values)

Use the table below to check the “Calculation” columns in student reports. Note that power is calculated in milliwatts (mW).

R_2 Value	Total R ($R_1 + R_2$)	Current i	Voltage v_{out}	Power P_{R_2}
2.2 k Ω	12.2 k Ω	0.820 mA	1.80 V	1.48 mW
4.7 k Ω	14.7 k Ω	0.680 mA	3.20 V	2.18 mW
10 k Ω	20.0 k Ω	0.500 mA	5.00 V	2.50 mW
20 k Ω	30.0 k Ω	0.333 mA	6.67 V	2.22 mW
33 k Ω	43.0 k Ω	0.233 mA	7.67 V	1.78 mW

Table 1: Theoretical values for Table 1. Measured values should be within resistor tolerance ($\approx 5\%$).

2 Part 2: LED Circuit Analysis

Theoretical Expectations

1. Forward Bias Behavior

- **Threshold:** An LED is a non-linear device. Current will remain near zero until the voltage across the LED reaches its **turn-on voltage** ($V_{turn-on}$).
- **Typical $V_{turn-on}$:** For a standard red LED, this is typically **1.8V – 2.0V**.
- **Behavior:**
 - **Input 1V:** Source < Turn-on. LED is OFF. $I \approx 0\text{mA}$. $V_{LED} \approx 1\text{V}$ (Open circuit behavior).
 - **Input 2V ~ 5V:** Source > Turn-on. LED turns ON. V_{LED} clamps near the forward voltage ($\approx 2\text{V}$) and rises very slowly.

Master Reference Table: Part 2 Measurements

The table below provides theoretical data for all permutations of R_1 and Input Voltage (V_{in}).
Note: Calculations assume a generic Red LED with $V_f \approx 1.8\text{V} - 2.0\text{V}$.

R_1 Value	Input (V_{in})	LED State	V_{LED} (approx)	V_{R1} (calc)	Current i (mA)
0 Ω	1.0 V	OFF	1.00 V	0.00 V	0.00
	2.0 V	Dim ON	1.80 V	0.00 V	0.05
	3.0 V	ON	1.88 V	0.00 V	0.29
	4.0 V	Bright	1.95 V	0.00 V	0.53
	5.0 V	Brightest	2.00 V	0.00 V	0.77
100 Ω	1.0 V	OFF	1.00 V	0.00 V	0.00
	2.0 V	Dim ON	1.80 V	0.01 V	0.05
	3.0 V	ON	1.88 V	0.03 V	0.28
	4.0 V	Bright	1.95 V	0.05 V	0.51
	5.0 V	Brightest	2.00 V	0.08 V	0.75
1 kΩ	1.0 V	OFF	1.00 V	0.00 V	0.00
	2.0 V	Faint	1.78 V	0.05 V	0.04
	3.0 V	ON	1.85 V	0.23 V	0.23
	4.0 V	ON	1.90 V	0.43 V	0.43
	5.0 V	Bright	1.95 V	0.62 V	0.62
100 kΩ	1.0 V	OFF	1.00 V	0.00 V	0.00
	2.0 V	OFF/Dim	1.60 V	0.38 V	0.004
	3.0 V	Very Dim	1.65 V	1.30 V	0.013
	4.0 V	Dim	1.70 V	2.21 V	0.022
	5.0 V	Dim	1.75 V	3.12 V	0.031

Table 2: Theoretical Measurements for LED Circuit (Figure 3).

TA Grading Notes

- **100 k Ω Behavior:** At this high resistance, current drops to $\approx 30 \mu\text{A}$. The LED may appear OFF or extremely faint. Most of the voltage drop occurs across R_1 , not the LED.
- **Low Voltage ($< 1.8\text{V}$):** If V_{in} is below the turn-on threshold, the circuit is open. $V_{LED} = V_{in}$ and $I = 0$.
- **Measurement Tolerance:** Student DMMs may not be sensitive enough to capture μA changes. Zero current readings at 100k Ω are acceptable for grading purposes.